

This question paper contains 4 printed pages]

Roll No.

--	--	--	--	--	--	--	--	--	--

S. No. of Question Paper : 6450

Unique Paper Code : 251301

D

Name of the Paper : Digital Electronics (ELHT-301)

Name of the Course : B.Sc. (H) Electronics

Semester : III

Duration : 3 Hours

Maximum Marks : 75

(Write your Roll No. on the top immediately on receipt of this question paper.)

Question number 1 is compulsory.

Attempt five questions in all.

Use of non-programmable scientific calculator is allowed.

1. (a) Convert 645.75_{10} into equivalent Binary, Octal and Hexadecimal number. 3
- (b) Find the complement of the following function and show that $f \cdot f' = 0$, where : 3
$$f = A + CD + (A + D')(C' + D)$$
- (c) Implement a full subtractor using 3 line to 8 line decoder. 3
- (d) Find the characteristic equation for SR flip-flop. 3
- (e) A memory has a capacity of $16 K \times 32$. Find : 3
 - (i) data input and data output lines
 - (ii) address lines
 - (iii) number of bytes.

P.T.O.

2. (a) Define Fan-in and Noise Margin. Explain working of positive logic CMOS NAND gate. 8
- (b) The seven bit hamming code as received is 0010001 (MSB as P_1 and LSB as D_7). Assuming that even parity has been used, check if it is correct or not. If not, then find the correct code. 3
- (c) Express the following functions in a sum of minterms and a product of maxterms : 4
- (i) $F(A, B, C) = (A' + B) (B' + C)$
- (ii) $F(X, Y, Z) = (XY + Y'Z)$
3. (a) Simplify the following function using Quine-Mc Cluskey method :

$$F(A, B, C, D) = \sum m (2, 3, 7, 10, 11, 14) + \sum d (1, 5, 15)$$
 Also verify the result using K-map. 7
- (b) Implement the following function using 4×1 MUX : 4

$$(x + y) (x' + z) (y + z')$$
- (c) Design a combinational circuit with three inputs x, y and z , and three outputs A, B and C. When the binary input is 0, 1, 2 or 3, the binary output is two greater than the input. When the binary input is 4, 5, 6 or 7, the binary output is two less than the input. 4

4. (a) Draw a schematic circuit of an edge triggered JK master slave flip-flop using NAND gates. Explain its operation with the help of a truth table. 6
- (b) The contents of a 8-bit bidirectional shift register are 11000011. What would be the contents of the register after two right shifts and then three left shifts. $D_{in} = 1$. 5
- (c) Multiply 1101_2 by 0111_2 using the computer method. 4
5. (a) Design a MOD-12 asynchronous counter using JK flip-flop. 6
- (b) Draw block diagram of four bit shift register with parallel input and serial output. 5
- (c) Using excitation table, convert a SR flip-flop to a D flip-flop. 4
6. (a) Design a type T-counter that goes through states : 8
- 6, 3, 7, 8, 2, 9, 1, 12, 14, 0, 6, 3

Also check for the bush. Give the state diagram, state table and circuit diagram.

- (b) Show that a Johnson's counter with three flip-flops produces a sequence of six states. Also sketch its waveforms. 4
- (c) What is a modulus of a counter ? A certain JK flip-flop has a $t_{pd} = 10$ ns. What is the largest Mod counter that can be constructed from these flip-flops and which will still operate up to 10 MHz. 3

P.T.O.

7. (a) Distinguish between SRAM and DRAM. Give the internal structure of single static RAM cell using MOS transistor and explain its working. 6
- (b) With the help of a block diagram explain the working of successive approximation ADC. 5
- (c) The logic levels used in a 6 bit R-2R ladder DAC are $1 = 5V$ and $0 = 0V$. What is the full scale output, percentage resolution and also find the output voltage for inputs : 4
- (i) 010110
- (ii) 101011